



Heaven's Light is Our Guide

**Department of Computer Science & Engineering**  
**Rajshahi University of Engineering & Technology, Bangladesh**

Course Code: CSE 2203  
Course Title: Digital Techniques

Date : 10.10.2017  
Session : VI  
Topic : Combinational Logic Circuits  
Faculty : Dr. Boshir Ahmed  
Professor  
Department of CSE, RUET  
E mail: boshir78@gmail.com

## Circuit Simplification Methods

- Boolean algebra: greatly depends on inspiration and experience.
- Karnaugh map: systematic, step-by-step approach.

## Algebraic Simplification

- Use the Boolean algebra theorems introduced in Lecture 4 to help simplify the expression for a logic circuit.
- Based on experience, often becomes a trial-and-error process.
- No easy way to tell whether a simplified expression is in its simplest form.

## Two Essential Steps

- The original expression is put into the sum-of-products form by repeated application of DeMorgan's theorem and multiplication of terms.
- The product terms are checked for common factors, and factoring is performed whenever possible.

## Examples 1-4

Original	Simplified
$ABC + AB'(A'C)'$	$A(B' + C)$
$ABC + ABC' + AB'C$	$A(B + C)$
$A'C(A'BD)' + A'BC'D' + AB'C$	$B'C + A'D'(B + C)$
$(A' + B)(A + B + D)D'$	$BD'$

## Examples 5-6

- $(A' + B)(A + B')$ : equivalent form  $A'B' + AB$
- $AB'C + A'BD + C'D'$ : cannot be simplified further.

## Analysis procedure

- To obtain the output Boolean functions from a logic diagram, proceed as follows:
  1. Label all gate outputs that are a function of input variables with arbitrary symbols. Determine the Boolean functions for each gate output.
  2. Label the gates that are a function of input variables and previously labeled gates with other arbitrary symbols. Find the Boolean functions for these gates.

## Analysis procedure

3. Repeat the process outlined in step 2 until the outputs of the circuit are obtained.
4. By repeated substitution of previously defined functions, obtain the output Boolean functions in terms of input variables.

## Example

$$F_2 = AB + AC + BC; \quad T_1 = A + B + C; \quad T_2 = ABC; \quad T_3 = F_2' T_1;$$

$$F_1 = T_3 + T_2$$

$$F_1 = T_3 + T_2 = F_2' T_1 + ABC = A'BC' + A'B'C + AB'C' + ABC$$

 


Fig. 4-2 Logic Diagram for Analysis Example

9

## Derive truth table from logic diagram

- We can derive the truth table in Table 4-1 by using the circuit of Fig.4-2.

**Table 4-1**  
Truth Table for the Logic Diagram of Fig. 4-2

A	B	C	F <sub>2</sub>	F <sub>2</sub>	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>	F <sub>1</sub>
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

## Design procedure

1. Table 4-2 is a Code-Conversion example, first, we can list the relation of the BCD and Excess-3 codes in the truth table.

**Table 4-2**  
*Truth Table for Code-Conversion Example*

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

11

## Designing Combinational Logic Circuits

1. Set up the truth table.
2. Write the AND term for each case where the output is a 1.
3. Write the sum-of-products expression for the output.
4. Simplify the output expression.
5. Implement the circuit for the final expression.

## Example 7

- Design a logic circuit that is to produce a HIGH output when the voltage (represented by a four-bit binary number ABCD) is greater than 6V.

## Example 8

- Four chairs A, B, C, and D are placed in a row. Each chair may be occupied ("1") or empty ("0"). A Boolean function F is ("1") if and only if there are two or more adjacent chairs that are empty.
  - a) Give the truth table defining the Boolean F.
  - b) Express F as a minterm expansion (standard sum of products).
  - c) Express F as a maxterm expansion (standard product of sums).
  - d) Simplify the minterm expansion of F.

## Karnaugh Map Method

- A graphical device to simplify a logic expression.
- Generally work on examples with up to 4 input variables.
- From truth table to logic expression to K map.

## Complete Simplification Process

- Step 1: Construct the K map and places 1s in those squares corresponding to the 1s in the truth table. Places 0s in the other squares.
- Step 2: Examine the map for adjacent 1s and loop those 1s which are not adjacent to any other 1s. (isolated 1s)
- Step 3: Look for those 1s which are adjacent to only one other 1. Loop any pair containing such a 1.
- Step 4: Loop any octet even when it contains some 1s that have already been looped.



## Complete Simplification Process

- Step 5: Loop any quad that contains one or more 1s that have not already been looped, making sure to use the minimum number of loops.
- Step 6: Loop any pairs necessary to include any 1s have not already been looped, making sure to use the minimum number of loops.
- Step 7: Form the ORed sum of all the terms generated by each loop.

## Filling K Map from Output Expression

- What to do when the desired output is presented as a Boolean expression instead of a truth table?
- Step 1: Convert the expression into SOP form.
- Step 2: For each product term in the SOP expression, place a 1 in each K-map square whose label contains the same combination of input values. Place a 0 in other squares.
- Example 9:  $y = C'(A'B'D' + D) + AB'C + D'$

## Don't-Care Conditions

- Some logic circuits can be designed so that there are certain input conditions for which there are no specified output levels.
- A circuit designer is free to make the output for any don't care condition either a 0 or a 1 in order to produce the simplest output expression.

## Karnaugh map

2. For each symbol of the Excess-3 code, we use 1's to draw the map for simplifying Boolean function.

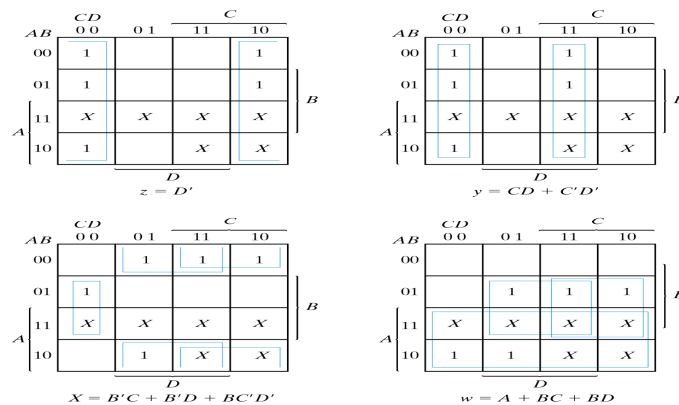


Fig. 4-3 Maps for BCD to Excess-3 Code Converter

## Circuit implementation

$$z = D'; \quad y = CD + C'D' = CD + (C + D)'$$

$$x = B'C + B'D + BC'D' = B'(C + D) + B(C + D)'$$

$$w = A + BC + BD = A + B(C + D)$$

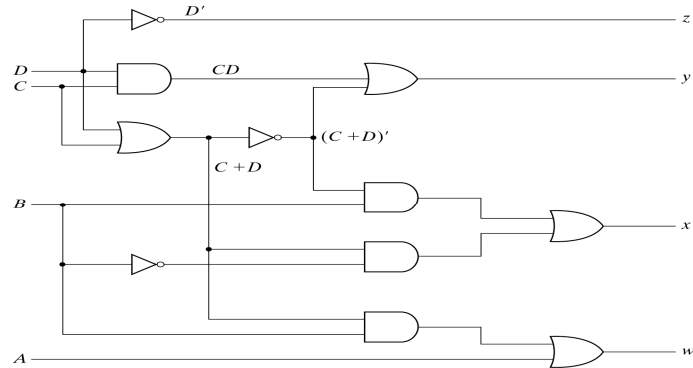


Fig. 4-4 Logic Diagram for BCD to Excess-3 Code Converter

21

## Binary Adder-Subtractor

- A combinational circuit that performs the addition of two bits is called a **half adder**.
- The truth table for the half adder is listed below:

**Table 4-3**  
*Half Adder*

<i>x</i>	<i>y</i>	<i>C</i>	<i>S</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

S: Sum  
C: Carry

$$S = x'y + xy'$$

$$C = xy$$

22

## Implementation of Half-Adder

 


Fig. 4-5 Implementation of Half-Adder

23

## Full-Adder

- One that performs the addition of three bits (two significant bits and a previous carry) is a **full adder**.

**Table 4-4**  
*Full Adder*

$x$	$y$	$z$	$C$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

24

## Simplified Expressions

 


Fig. 4-6 Maps for Full Adder

$$S = x'y'z + x'yz' + xy'z' + xyz$$

$$C = xy + xz + yz$$

25

## Full adder implemented in SOP

 


Fig. 4-7 Implementation of Full Adder in Sum of Products

26

## Another implementation

- Full-adder can also implemented with **two half adders** and **one OR gate** (Carry Look-Ahead adder).

$$\begin{aligned}
 S &= z \oplus (x \oplus y) \\
 &= z'(xy' + x'y) + z(xy' + x'y) \\
 &= xy'z' + x'yz' + xyz + x'y'z \\
 C &= z(xy' + x'y) + xy = xy'z + x'yz + xy
 \end{aligned}$$

 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

27

## Binary adder

- This is also called **Ripple Carry Adder**, because of the construction with full adders are connected in cascade.

Subscript i:	3	2	1	0	
Input carry	0	1	1	0	$C_i$
Augend	1	0	1	1	$A_i$
Addend	0	0	1	1	$B_i$
Sum	1	1	1	0	$S_i$
Output carry	0	0	1	1	$C_{i+1}$

 


Fig. 4-9 4-Bit Adder

## Carry Propagation

- Fig.4-9 causes a **unstable** factor on **carry bit**, and produces a **longest propagation delay**.
- The signal from  $C_i$  to the output carry  $C_{i+1}$ , **propagates through an AND and OR gates**, so, for an n-bit RCA, there are  **$2n$**  gate levels for the carry to propagate from input to output.

29

## Carry Propagation

- Because the propagation delay will affect the output signals on different time, so the signals are **given enough time to get the precise and stable outputs**.
- The most widely used technique employs the principle of **carry look-ahead** to **improve the speed of the algorithm**.

 


Fig. 4-10 Full Adder with P and G Shown

30

## Boolean functions

$$P_i = A_i \oplus B_i \quad \text{steady state value}$$

$$G_i = A_i B_i \quad \text{steady state value}$$

Output sum and carry

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

$G_i$  : carry generate

$P_i$  : carry propagate

$C_0$  = input carry

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

- $C_3$  does not have to wait for  $C_2$  and  $C_1$  to propagate.

31

## Logic diagram of carry look-ahead generator

- $C_3$  is propagated at the same time as  $C_2$  and  $C_1$ .

 


Fig. 4-11 Logic Diagram of Carry Lookahead Generator

32



## 4-bit adder with carry lookahead

- Delay time of n-bit CLAA = XOR + (AND + OR) + XOR

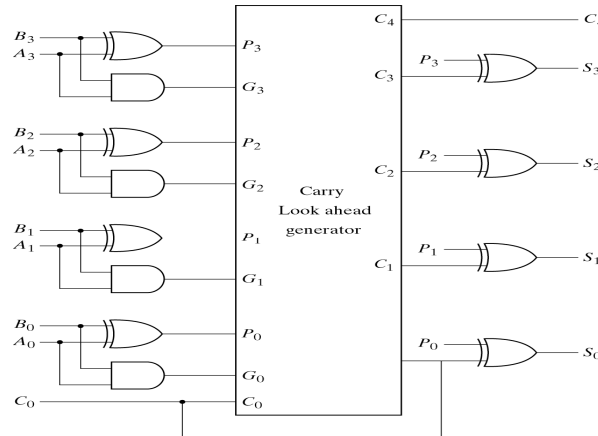


Fig. 4-12 4-Bit Adder with Carry Lookahead

33

## Binary subtractor

$M = 1 \rightarrow \text{subtractor}$  ;  $M = 0 \rightarrow \text{adder}$

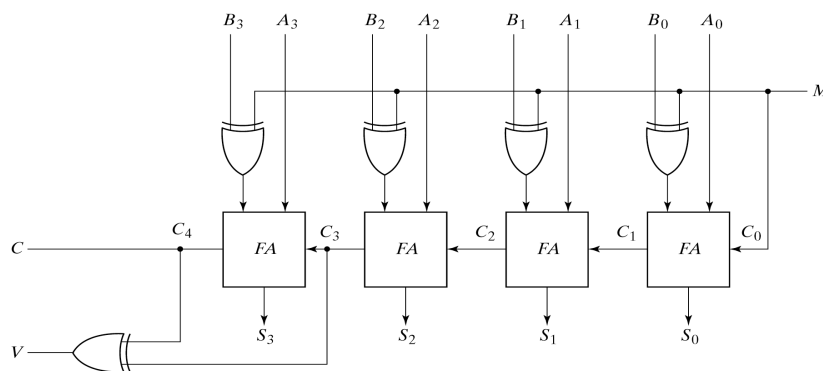


Fig. 4-13 4-Bit Adder Subtractor

34

## Rules of BCD adder

- When the binary sum is **greater than 1001**, we obtain a **non-valid BCD** representation.
- The **addition of binary 6(0110)** to the binary sum **converts it to the correct BCD** representation and also produces an output carry as required.
- To distinguish them from binary 1000 and 1001, which also have a 1 in position  $Z_8$ , we specify further that either  $Z_4$  or  $Z_2$  must have a 1.

$$C = K + Z_8Z_4 + Z_8Z_2$$

35

## Implementation of BCD adder

- A decimal parallel adder that adds  $n$  decimal digits needs  $n$  BCD adder stages.
- The **output carry from one stage** must be **connected** to the input carry of the next higher-order stage.

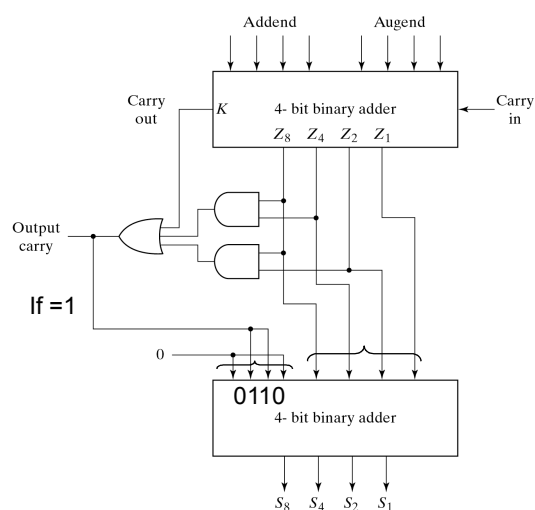


Fig. 4-14 Block Diagram of a BCD Adder

## Binary multiplier

- Usually there are **more bits** in the partial products and it is necessary to use **full adders** to produce the sum of the partial products.

 


Fig. 4-15 2-Bit by 2-Bit Binary Multiplier

37

## 4-bit by 3-bit binary multiplier

- For **J multiplier** bits and **K multiplicand** bits we need **(J X K)** AND gates and **(J - 1) K-bit adders** to produce a product of J+K bits.
- K=4 and J=3, we need 12 AND gates and two 4-bit adders.

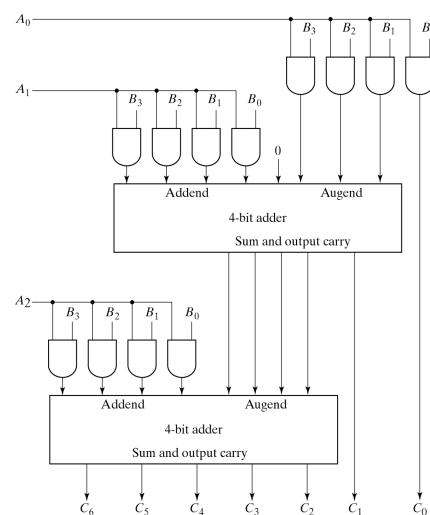



Fig. 4-16 4-Bit by 3-Bit Binary Multiplier

## Decoders

- The decoder is called n-to-m-line decoder, where  $m \leq 2^n$ .
- the decoder is also used in conjunction with other code converters such as a BCD-to-seven\_segment decoder.
- 3-to-8 line decoder: For each possible input combination, there are seven outputs that are equal to 0 and only one that is equal to 1.

39

## Implementation and truth table

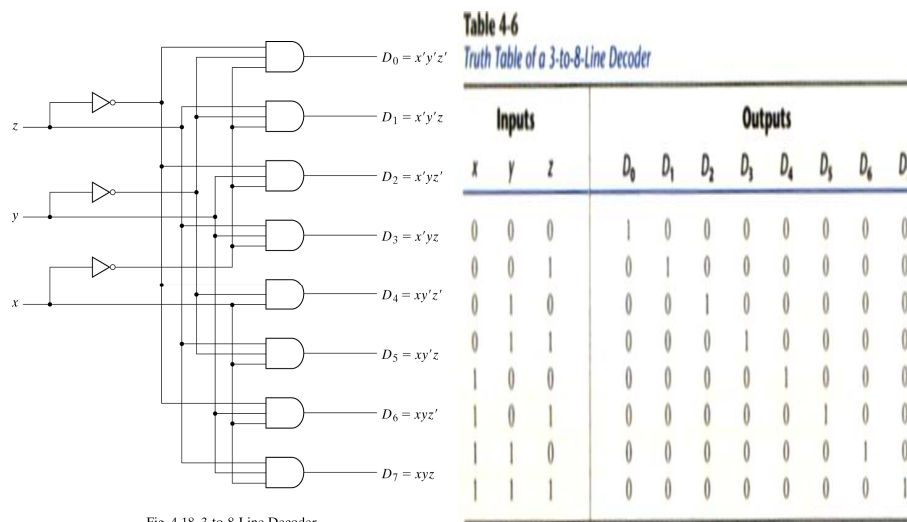

40

## Decoder with enable input

- Some decoders are constructed with NAND gates, it becomes more economical to generate the decoder minterms in their complemented form.
- As indicated by the truth table, only one output can be equal to 0 at any given time, all other outputs are equal to 1.


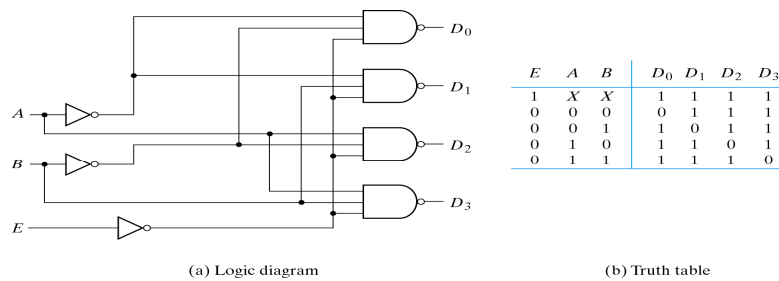


Fig. 4-19 2-to-4-Line Decoder with Enable Input

41
 
## Demultiplexer

- A decoder with an enable input is referred to as a decoder/demultiplexer.
- The truth table of demultiplexer is the same with decoder.



42

## 3-to-8 decoder with enable implement the 4-to-16 decoder

 


Fig. 4-20  $4 \times 16$  Decoder Constructed with Two  $3 \times 8$  Decoders

43

## Implementation of a Full Adder with a Decoder

- From table 4-4, we obtain the functions for the combinational circuit in sum of minterms:

$$S(x, y, z) = \sum(1, 2, 4, 7)$$

$$C(x, y, z) = \sum(3, 5, 6, 7)$$

 


Fig. 4-21 Implementation of a Full Adder with a Decoder

44

## Encoders

- An **encoder** is the **inverse operation of a decoder**.
- We can derive the Boolean functions by table 4-7

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

**Table 4-7**  
*Truth Table of Octal-to-Binary Encoder*

Inputs								Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	$x$	$y$	$z$
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

## Priority encoder

- If two **inputs** are **active simultaneously**, the **output** produces an **undefined combination**. We can establish an input **priority** to ensure that only one input is encoded.
- Another ambiguity** in the octal-to-binary encoder is that an **output with all 0's** is generated when **all the inputs are 0**; the output is the same as when  $D_0$  is equal to 1.
- The discrepancy tables on Table 4-7 and Table 4-8 can **resolve aforesaid condition by providing one more output** to indicate that at least one input is equal to 1.

## Priority encoder

$V=0 \rightarrow$  no valid inputs

$V=1 \rightarrow$  valid inputs

$X$ 's in output columns represent

don't-care conditions

$X$ 's in the input columns are useful for representing a truth table in condensed form.

Instead of listing all 16

minterms of four variables.

**Table 4-8**  
Truth Table of a Priority Encoder

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$x$	$y$	$V$
0	0	0	0	$X$	$X$	0
1	0	0	0	0	0	1
$X$	1	0	0	0	1	1
$X$	$X$	1	0	1	0	1
$X$	$X$	$X$	1	1	1	1

47

## 4-input priority encoder

- Implementation of table 4-8

$$x = D_2 + D_3$$

$$y = D_3 + D_1 D'_2$$

$$V = D_0 + D_1 + D_2 + D_3$$

 


Fig. 4-22 Maps for a Priority Encoder

 


Fig. 4-23 4-Input Priority Encoder

48



## Multiplexers


$$S = 0, Y = I_0$$

$$S = 1, Y = I_1$$


Truth Table →

S	Y
0	$I_0$
1	$I_1$

$$Y = S'I_0 + SI_1$$

 

(a) Logic diagram

 


(b) Block diagram

Fig. 4-24 2-to-1-Line Multiplexer

49

## 4-to-1 Line Multiplexer

 

(a) Logic diagram

$s_1$	$s_0$	Y
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

(b) Function table

Fig. 4-25 4-to-1-Line Multiplexer

50

## Quadruple 2-to-1 Line Multiplexer

- Multiplexer circuits can be combined with common selection inputs to provide multiple-bit selection logic. Compare with Fig4-24.

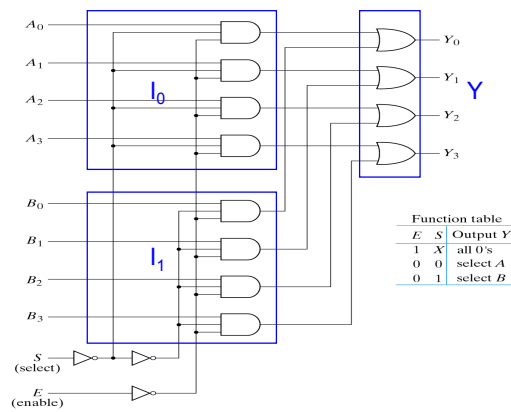


Fig. 4-26 Quadruple 2-to-1-Line Multiplexer

51


## Boolean function implementation

- A more efficient method for implementing a Boolean function of n variables with a multiplexer that has n-1 selection inputs.

$$F(x, y, z) = \Sigma(1, 2, 6, 7)$$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

(a) Truth table

 

(b) Multiplexer implementation

Fig. 4-27 Implementing a Boolean Function with a Multiplexer

52

## 4-input function with a multiplexer

$$F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$$

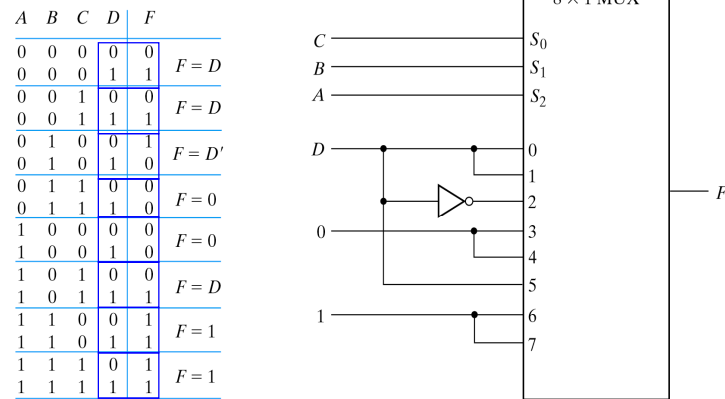


Fig. 4-28 Implementing a 4-Input Function with a Multiplexer

53

Thank You

Next topic