



Heaven's Light is Our Guide


**Department of Computer Science & Engineering**  
**Rajshahi University of Engineering & Technology, Bangladesh**

Course Code: CSE 2203  
Course Title: Digital Techniques

Date : 20.09.2017  
Session : V  
Topic : Gate Level Minimization  
Faculty : Dr. Boshir Ahmed  
Professor  
Department of CSE, RUET  
E mail: boshir78@gmail.com
 
## Combinational Logic Circuit from Logic Function

- Consider function  $F = A' + B \cdot C' + A' \cdot B'$
- A combinational logic circuit can be constructed to implement F, by appropriately connecting input signals and logic gates:
  - Circuit input signals → from function variables (A, B, C)
  - Circuit output signal → function output (F)
  - Logic gates → from logic operations




## Combinational Logic Circuit from Logic Function (cont.)

- In order to design a cost-effective and efficient circuit, we must minimize the circuit's size (area) and propagation delay (time required for an input signal change to be observed at the output line)
- Observe the truth table of  $F=A' + B \cdot C'$  +  $A' \cdot B'$  and  $G=A' + B \cdot C'$
- Truth tables for F and G are identical  
→ same function
- Use G to implement the logic circuit (less components)

A	B	C	F	G
0	0	0	1	1
0	0	1	1	1
0	1	0	1	1
0	1	1	1	1
1	0	0	0	0
1	0	1	0	0
1	1	0	1	1
1	1	1	0	0
 
## Combinational Logic Circuit from Logic Function (cont.)



## Boolean expressions-NOT unique

- Unlike truth tables, expressions representing a Boolean function are NOT unique.
- Example:
  - $F(x,y,z) = x' \cdot y' \cdot z' + x' \cdot y \cdot z' + x \cdot y \cdot z'$
  - $G(x,y,z) = x' \cdot y' \cdot z' + y \cdot z'$
- The corresponding truth tables for  $F()$  and  $G()$  are to the right. They are identical.
- Thus,  $F() = G()$

x	y	z	F	G
0	0	0	1	1
0	0	1	0	0
0	1	0	1	1
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	1	1
1	1	1	0	0

## Algebraic Manipulation

- Boolean algebra is a useful tool for simplifying digital circuits.
- Why do it? Simpler can mean cheaper, smaller, faster.
- Example: Simplify  $F = x'yz + x'yz' + xz$ .
 
$$\begin{aligned}
 F &= x'yz + x'yz' + xz \\
 &= x'y(z+z') + xz \\
 &= x'y \cdot 1 + xz \\
 &= x'y + xz
 \end{aligned}$$

## Algebraic Manipulation (cont.)

- Example: Prove

$$x'y'z' + x'yz' + xyz' = x'z' + yz'$$

- **Proof:**

$$\begin{aligned} x'y'z' + x'yz' + xyz' &= x'y'z' + x'yz' + x'yz' + xyz' \\ &= x'z'(y' + y) + yz'(x' + x) \\ &= x'z' \cdot 1 + yz' \cdot 1 \\ &= x'z' + yz' \end{aligned}$$

## Complement of a Function

- The complement of a function is derived by interchanging ( $\cdot$  and  $+$ ), and (1 and 0), and complementing each variable.
- Otherwise, interchange 1s to 0s in the truth table column showing F.
- The *complement* of a function IS NOT THE SAME as the *dual* of a function.

## Complementation: Example

- Find  $G(x,y,z)$ , the complement of  $F(x,y,z) = xy'z' + x'yz$
- $G = F' = (xy'z' + x'yz)'$   
 $= (xy'z')' \cdot (x'yz)'$  *DeMorgan*  
 $= (x'+y+z) \cdot (x+y'+z')$  *DeMorgan* again
- Note: The complement of a function can also be derived by finding the function's *dual*, and then complementing all of the literals

## Canonical and Standard Forms

- We need to consider formal techniques for the simplification of Boolean functions.
  - Identical functions will have exactly the same canonical form.
  - Minterms and Maxterms
  - Sum-of-Minterms and Product-of- Maxterms
  - Product and Sum terms
  - Sum-of-Products (SOP) and Product-of-Sums (POS)

## Definitions

- *Literal*: A variable or its complement
- *Product term*: literals connected by •
- *Sum term*: literals connected by +
- *Minterm*: a product term in which all the variables appear exactly once, either complemented or uncomplemented
- *Maxterm*: a sum term in which all the variables appear exactly once, either complemented or uncomplemented

## Minterm

- Represents exactly one combination in the truth table.
- Denoted by  $m_j$ , where  $j$  is the decimal equivalent of the minterm's corresponding binary combination ( $b_j$ ).
- A variable in  $m_j$  is complemented if its value in  $b_j$  is 0, otherwise is uncomplemented.
- Example: Assume 3 variables (A,B,C), and  $j=3$ . Then,  $b_j = 011$  and its corresponding minterm is denoted by  $m_j = A'BC$

## Maxterm

- Represents exactly one combination in the truth table.
- Denoted by  $M_j$ , where  $j$  is the decimal equivalent of the maxterm's corresponding binary combination ( $b_j$ ).
- A variable in  $M_j$  is complemented if its value in  $b_j$  is 1, otherwise is uncomplemented.
- Example: Assume 3 variables (A,B,C), and  $j=3$ . Then,  $b_j = 011$  and its corresponding maxterm is denoted by  $M_j = A+B'+C'$

## Truth Table notation for Minterms and Maxterms

- Minterms and Maxterms are easy to denote using a truth table.
- Example:  
Assume 3 variables x,y,z (order is fixed)

x	y	z	Minterm	Maxterm
0	0	0	$x'y'z' = m_0$	$x+y+z = M_0$
0	0	1	$x'y'z = m_1$	$x+y+z' = M_1$
0	1	0	$x'yz' = m_2$	$x+y'+z = M_2$
0	1	1	$x'yz = m_3$	$x+y'+z' = M_3$
1	0	0	$xy'z' = m_4$	$x'+y+z = M_4$
1	0	1	$xy'z = m_5$	$x'+y+z' = M_5$
1	1	0	$xyz' = m_6$	$x'+y'+z = M_6$
1	1	1	$xyz = m_7$	$x'+y'+z' = M_7$

## Canonical Forms (Unique)

- Any Boolean function  $F()$  can be expressed as a *unique* **sum** of **minterms** and a unique **product** of **maxterms** (under a fixed variable ordering).
- In other words, every function  $F()$  has two canonical forms:
  - Canonical Sum-Of-Products (sum of minterms)
  - Canonical Product-Of-Sums (product of maxterms)

## Canonical Forms (cont.)

- Canonical Sum-Of-Products:  
The minterms included are those  $m_j$  such that  $F() = 1$  in row  $j$  of the truth table for  $F()$ .
- Canonical Product-Of-Sums:  
The maxterms included are those  $M_j$  such that  $F() = 0$  in row  $j$  of the truth table for  $F()$ .



## Example

- Truth table for  $f_1(a,b,c)$  at right
- The canonical sum-of-products form for  $f_1$  is  

$$f_1(a,b,c) = m_1 + m_2 + m_4 + m_6$$

$$= a'b'c + a'bc' + ab'c' + abc'$$
- The canonical product-of-sums form for  $f_1$  is  

$$f_1(a,b,c) = M_0 \cdot M_3 \cdot M_5 \cdot M_7$$

$$= (a+b+c) \cdot (a+b'+c') \cdot (a'+b+c') \cdot (a'+b'+c')$$
- Observe that:  $m_j = M_j'$

a	b	c	$f_1$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

## Shorthand: $\Sigma$ and $\Pi$

- $f_1(a,b,c) = \Sigma m(1,2,4,6)$ , where  $\Sigma$  indicates that this is a sum-of-products form, and  $m(1,2,4,6)$  indicates that the minterms to be included are  $m_1$ ,  $m_2$ ,  $m_4$ , and  $m_6$ .
- $f_1(a,b,c) = \Pi M(0,3,5,7)$ , where  $\Pi$  indicates that this is a product-of-sums form, and  $M(0,3,5,7)$  indicates that the maxterms to be included are  $M_0$ ,  $M_3$ ,  $M_5$ , and  $M_7$ .
- Since  $m_j = M_j'$  for any  $j$ ,  

$$\Sigma m(1,2,4,6) = \Pi M(0,3,5,7) = f_1(a,b,c)$$

## Conversion Between Canonical Forms

- Replace  $\sum$  with  $\prod$  (or *vice versa*) and replace those  $j$ 's that appeared in the original form with those that do not.

- Example:

$$\begin{aligned}
 f_1(a,b,c) &= a'b'c + a'bc' + ab'c' + abc' \\
 &= m_1 + m_2 + m_4 + m_6 \\
 &= \sum(1,2,4,6) \\
 &= \prod(0,3,5,7) \\
 &= (a+b+c) \cdot (a+b'+c') \cdot (a'+b+c') \cdot (a'+b'+c')
 \end{aligned}$$

## Standard Forms (NOT Unique)

- Standard forms are “*like*” canonical forms, except that not all variables need appear in the individual product (SOP) or sum (POS) terms.
- Example:  
 $f_1(a,b,c) = a'b'c + bc' + ac'$   
 is a *standard* sum-of-products form
- $f_1(a,b,c) = (a+b+c) \cdot (b'+c') \cdot (a'+c')$   
 is a *standard* product-of-sums form.

## Conversion of SOP from standard to canonical form

- Expand *non-canonical* terms by inserting equivalent of 1 in each missing variable x:  
 $(x + x') = 1$
- Remove duplicate minterms
- $f_1(a,b,c) = a'b'c + bc' + ac'$   
 $= a'b'c + (a+a')bc' + a(b+b')c'$   
 $= a'b'c + abc' + a'bc' + abc' + ab'c'$   
 $= a'b'c + abc' + a'bc + ab'c'$


## Conversion of POS from standard to canonical form

- Expand noncanonical terms by adding 0 in terms of missing variables (e.g.,  $xx' = 0$ ) and using the distributive law
- Remove duplicate maxterms
- $f_1(a,b,c) = (a+b+c) \cdot (b'+c') \cdot (a'+c')$   
 $= (a+b+c) \cdot (aa'+b'+c') \cdot (a'+bb'+c')$   
 $= (a+b+c) \cdot (a+b'+c') \cdot (a'+b'+c') \cdot (a'+b+c')$   
 $= (a+b+c) \cdot (a+b'+c') \cdot (a'+b'+c') \cdot (a'+b+c')$

## Karnaugh Maps

- Karnaugh maps (K-maps) are *graphical* representations of boolean functions.
- One **map cell** corresponds to a row in the truth table.
- Also, one map cell corresponds to a minterm or a maxterm in the boolean expression
- Multiple-cell areas of the map correspond to standard terms.

## Two-Variable Map

 

NOTE: ordering of variables is IMPORTANT for  $f(x_1, x_2)$ ,  $x_1$  is the row,  $x_2$  is the column.

Cell 0 represents  $x_1'x_2'$ ; Cell 1 represents  $x_1'x_2$ ; etc. If a minterm is present in the function, then a 1 is placed in the corresponding cell.

## Two-Variable Map (cont.)

- Any two adjacent cells in the map differ by ONLY one variable, which appears complemented in one cell and uncomplemented in the other.
- Example:  
 $m_0 (=x_1'x_2')$  is adjacent to  $m_1 (=x_1'x_2)$  and  $m_2 (=x_1x_2')$  but NOT  $m_3 (=x_1x_2)$

## 2-Variable Map -- Example

- $$f(x_1, x_2) = x_1'x_2' + x_1'x_2 + x_1x_2'$$

$$= m_0 + m_1 + m_2$$


$$= x_1' + x_2'$$
- 1s placed in K-map for specified minterms  $m_0, m_1, m_2$
- Grouping (ORing) of 1s allows simplification
- What (simpler) function is represented by each dashed rectangle?
  - $x_1' = m_0 + m_1$
  - $x_2' = m_0 + m_2$
- Note  $m_0$  covered twice

		$x_2$	
		0	1
$x_1$	0	0	1
	1	2	3

## Minimization as SOP using K-map

- Enter 1s in the K-map for each product term in the function
- Group *adjacent* K-map cells containing 1s to obtain a product with fewer variables. Group size must be in power of 2 (2, 4, 8, ...)
- Handle “boundary wrap” for K-maps of 3 or more variables.
- Realize that answer may not be unique

## Three-Variable Map

 


-Note: variable ordering is (x,y,z); yz specifies column, x specifies row.

-Each cell is adjacent to **three** other cells (left or right or top or bottom or edge wrap)

 
## Three-Variable Map (cont.)

The types of structures that are either minterms or are generated by repeated application of the minimization theorem on a three variable map are shown at right. Groups of 1, 2, 4, 8 are possible.


 
## Simplification

- Enter minterms of the Boolean function into the map, then group terms
- Example:  $f(a,b,c) = a'c + abc + bc'$
- Result:  $f(a,b,c) = a'c + b$



## More Examples

- $f_1(x, y, z) = \sum m(2,3,5,7)$

- $f_1(x, y, z) = x'y + xz$

x \ yz				
	00	01	11	10
0			1	1
1		1	1	


- $f_2(x, y, z) = \sum m(0,1,2,3,6)$

- $f_2(x, y, z) = x' + yz'$

1	1	1	1
			1

## Four-Variable Maps

wx \ yz				
	00	01	11	10
00	$m_0$	$m_1$	$m_3$	$m_2$
01	$m_4$	$m_5$	$m_7$	$m_6$
11	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
10	$m_8$	$m_9$	$m_{11}$	$m_{10}$

 

- Top cells are adjacent to bottom cells. Left-edge cells are adjacent to right-edge cells.
- Note variable ordering (WXYZ).



## Four-variable Map Simplification

- One square represents a minterm of 4 literals.
- A rectangle of 2 adjacent squares represents a product term of 3 literals.
- A rectangle of 4 squares represents a product term of 2 literals.
- A rectangle of 8 squares represents a product term of 1 literal.
- A rectangle of 16 squares produces a function that is equal to logic 1.

## Example

- Simplify the following Boolean function  
 $(A,B,C,D) = \sum m(0,1,2,4,5,7,8,9,10,12,13)$ .
- First put the function  $g( )$  into the map, and then group as many 1s as possible.

ab \ cd				
	1	1		1
	1	1	1	
	1	1		
	1	1		1

1	1		1
1	1	1	
1	1		
1	1		1

$$g(A,B,C,D) = c' + b'd' + a'bd$$

## Don't Care Conditions

- There may be a combination of input values which
  - will **never** occur
  - if they do occur, the output is of no concern.
- The function value for such combinations is called a *don't care*.
- They are denoted with **x** or **–**. Each **x** may be arbitrarily assigned the value 0 or 1 in an implementation.
- Don't cares can be used to **further** simplify a function

## Example

- Simplify the function  $f(a,b,c,d)$  whose K-map is shown at the right.
- $f = a'c'd + ab' + cd' + a'bc'$   
or
- $f = a'c'd + ab' + cd' + a'bd'$

		cd			
		00	01	11	10
ab	00	0	1	0	1
	01	1	1	0	1
	11	0	0	x	x
	10	1	1	x	x

0	1	0	1
1	1	0	1
0	0	x	x
1	1	x	x

0	1	0	1
1	1	0	1
0	0	x	x
1	1	x	x

## Another Example


- Simplify the function  $g(a,b,c,d)$  whose K-map is shown at right.
- $g = a'c' + ab$   
or
- $g = a'c' + b'd$

		cd			
ab	x	1	0	0	
	1	x	0	x	
	1	x	x	1	
	0	x	x	0	

x	1	0	0
1	x	0	x
1	x	x	1
0	x	x	0

x	1	0	0
1	x	0	x
1	x	x	1
0	x	x	0


## AND-OR (SOP) Emulation Using NANDs

 

Two-level implementations

- a) Original SOP
- b) Implementation with NANDs
 
## AND-OR (SOP) Emulation Using NANDs (cont.)




Verify:

(a)  $G = WXY + YZ$

(b)  $G = ((WXY)' \cdot (YZ)')'$   
 $= (WXY)'' + (YZ)'' = WXY + YZ$

## SOP with NAND

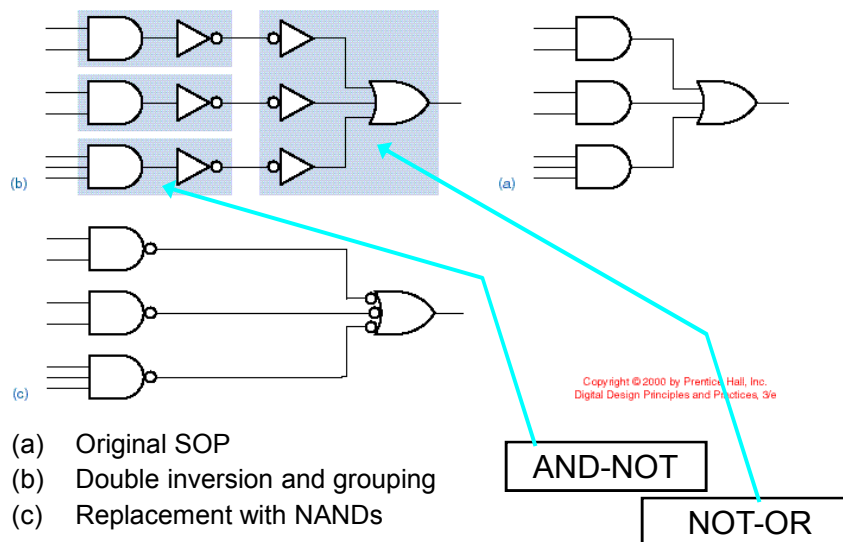


## Two-Level NAND Gate Implementation - Example

$$F(X,Y,Z) = \sum m(0,6)$$

1. Express F in SOP form:  
 $F = X'Y'Z' + XYZ'$
2. Obtain the AND-OR implementation for F.
3. Add bubbles and inverters to transform AND-OR to NAND-NAND gates.

### Example (cont.)

 

Two-level implementation with NANDs  
 $F = X'Y'Z' + XYZ'$

## Multilevel NAND Circuits

Starting from a multilevel circuit:

1. Convert all AND gates to NAND gates with AND-NOT graphic symbols.
2. Convert all OR gates to NAND gates with NOT-OR graphic symbols.
3. Check all the bubbles in the diagram. For every bubble that is not counteracted by another bubble along the same line, insert a NOT gate or complement the input literal from its original appearance.

### Example

Use NAND gates and NOT gates to implement


$$Z = E'F(AB + C' + D') + GH$$

AB


AB + C' + D'

E'F(AB + C' + D')


E'F(AB + C' + D') + GH

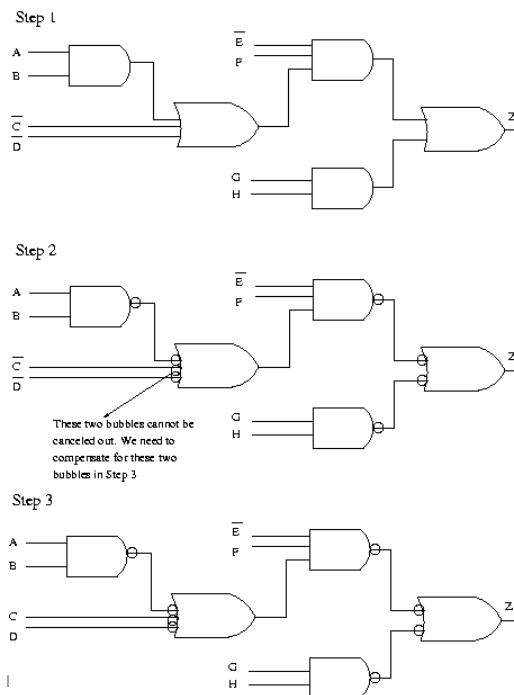

## Yet Another Example!

 

(a) AND – OR gates

 

(b) NAND gates

Fig. 2-32 Implementing  $F = (A \bar{B} + \bar{A} B) E (C + \bar{D})$

## Two-Level NOR Gate Implementation - Example

$$F(X,Y,Z) = \sum m(0,6)$$


- Express  $F'$  in SOP form:

$$\begin{aligned} 1. \quad F' &= \sum m(1,2,3,4,5,7) \\ &= X'Y'Z + X'YZ' + X'YZ + XY'Z' + XY'Z + XYZ \end{aligned}$$

$$2. \quad F' = XY' + X'Y + Z$$

- Take the complement of  $F'$  to get  $F$  in the POS form:  $F = (F')' = (X' + Y)(X + Y')Z'$
- Obtain the OR-AND implementation for  $F$ .
- Add bubbles and inverters to transform OR-AND implementation to NOR-NOR implementation.

## Example (cont.)

 


Two-level implementation with NORs

$$F = (F')' = (X' + Y)(X + Y')Z'$$
 
## Simplifying Logic Circuits (Practice)

- The circuits shown provide the same output
  - Circuit (b) is clearly less complex.




Logic circuits can be simplified using Boolean algebra and Karnaugh mapping.



## Algebraic Simplification

Simplify the logic circuit shown.

 


The first step is to determine the expression for the output:  $z = ABC + \overline{A}B(\overline{A}\overline{C})$

Once the expression is determined, break down large inverter signs by DeMorgan's theorems & multiply out all terms.

$$\begin{aligned}
 z &= ABC + \overline{A}B(\overline{A} + \overline{C}) && [\text{theorem (17)}] \\
 &= ABC + \overline{A}B(A + C) && [\text{cancel double inversions}] \\
 &= ABC + \overline{A}BA + \overline{A}BC && [\text{multiply out}] \\
 &= ABC + \overline{A}B + \overline{A}BC && [A \cdot A = A]
 \end{aligned}$$

## Algebraic Simplification

Simplify the logic circuit shown.

 

Factoring—the first & third terms above have **AC** in common, which can be factored out:

$$z = AC(B + \overline{B}) + \overline{A}B$$


Since  $B + \overline{B} = 1$ , then...

$$\begin{aligned}
 z &= AC(1) + \overline{A}B \\
 &= AC + \overline{A}B
 \end{aligned}$$

Factor out **A**, which results in...

## Algebraic Simplification

**Simplified logic circuit.**

 


$$z = A(C + \bar{B})$$

## Designing Combinational Logic Circuits

- To solve any logic design problem:
  - Interpret the problem and set up its truth table.
  - Write the **AND** (product) term for each case where output = 1.
  - Combine the terms in SOP form.
  - Simplify the output expression if possible.
  - Implement the circuit for the final, simplified expression.


**Circuit that produces a 1 output only for the A = 0, B = 1 condition.**

A	B	x
0	0	0
0	1	1
1	0	0
1	1	0

 
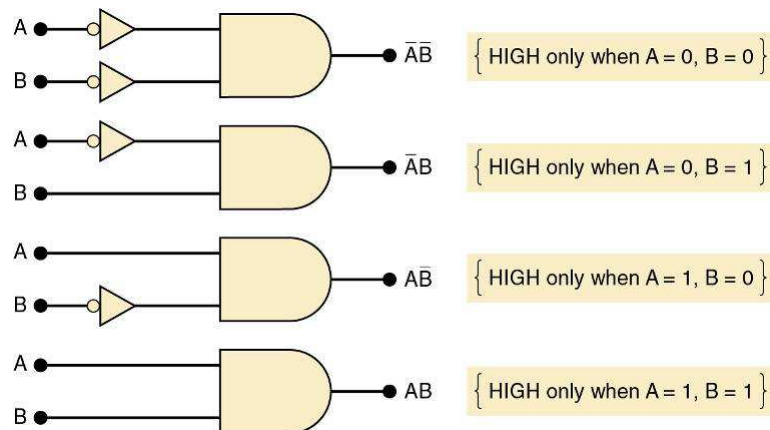
## Designing Combinational Logic Circuits


An **AND** gate with appropriate inputs can be used to produce a HIGH output for a specific set of input levels.


 
## Designing Combinational Logic Circuits

Each set of input conditions that is to produce a 1 output is implemented by a separate **AND** gate.

The **AND** outputs are **OR**ed to produce the final output.



## Designing Combinational Logic Circuits

### Truth table for a 3-input circuit.

A	B	C	x
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

**AND** terms for each case where output is 1.

$\rightarrow \bar{A}BC$   
 $\rightarrow \bar{A}BC$   
 $\rightarrow ABC$

## Designing Combinational Logic Circuits

Design a logic circuit with three inputs, A, B, and C. Output to be HIGH only when a majority inputs are HIGH.

Truth table.

A	B	C	x
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

**AND** terms for each case where output is 1.

$\rightarrow \bar{A}BC$   
 $\rightarrow A\bar{B}C$   
 $\rightarrow AB\bar{C}$   
 $\rightarrow ABC$

**SOP expression for the output:**

$$x = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

## Designing Combinational Logic Circuits


**Design a logic circuit with three inputs, A, B, and C. Output to be HIGH only when a majority inputs are HIGH.**

Simplified output expression:

$$x = ABC + ABC + ABC + ABC + ABC + ABC$$

Implementing the circuit after factoring:


$$x = BC + AC + AB$$

 

Since the expression is in SOP form, the circuit is a group of **AND** gates, working into a single **OR** gate.



## Exclusive OR and Exclusive NOR Circuits

 **Truth table and circuit for detecting equality of two-bit binary numbers.**



$x_1$	$x_0$	$y_1$	$y_0$	$z$ (Output)
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1
  
## Exclusive OR and Exclusive NOR Circuits



Thank You

Next topic